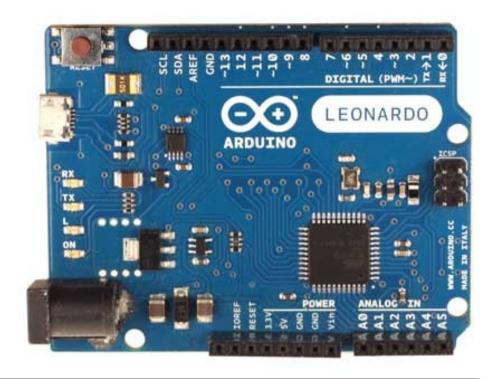
Welcome! This tutorial is designed to teach you the basics of making your own electronic circuits using the Arduino microcontroller, the blue thing on the right. You will learn how to safely connect different kinds of components to the Arduino and how to program it to interact with the outside world.










We will be using several different electronic components with the Arduino. Can you name the ones pictured on the page?

Don't worry if you have never programmed an Arduino before, it's the easiest thing in the world!

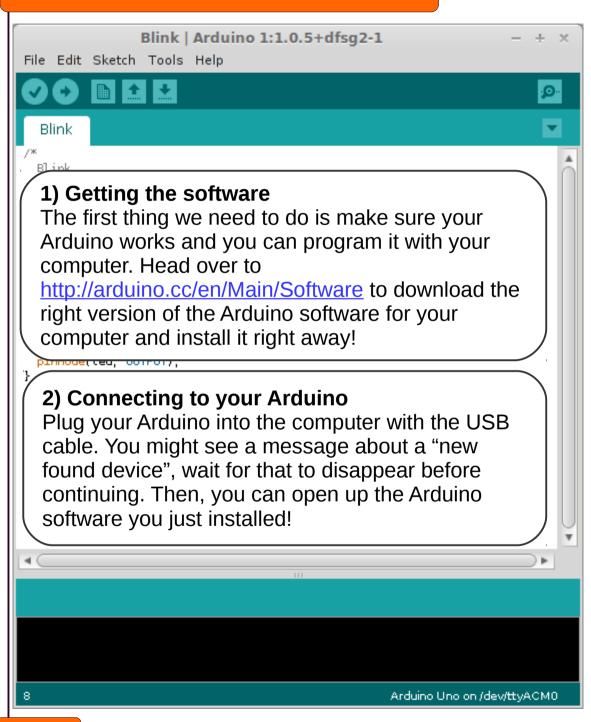Have a look at: http://arduino.cc/en/Tutorial





3) Load An Example Program

When the software opens, click on: File -> Examples -> 01 Basics -> Blink. You will see another window open with some example code. Don't worry if you don't understand yet, we'll get to that!


4) Configure your board

We are using an "Arduino Leonardo". So under Tools -> Board Select the Arduino Leonardo! You will also need to select the right "port" under Tools -> Port. It is usually the one with the biggest number at the end!

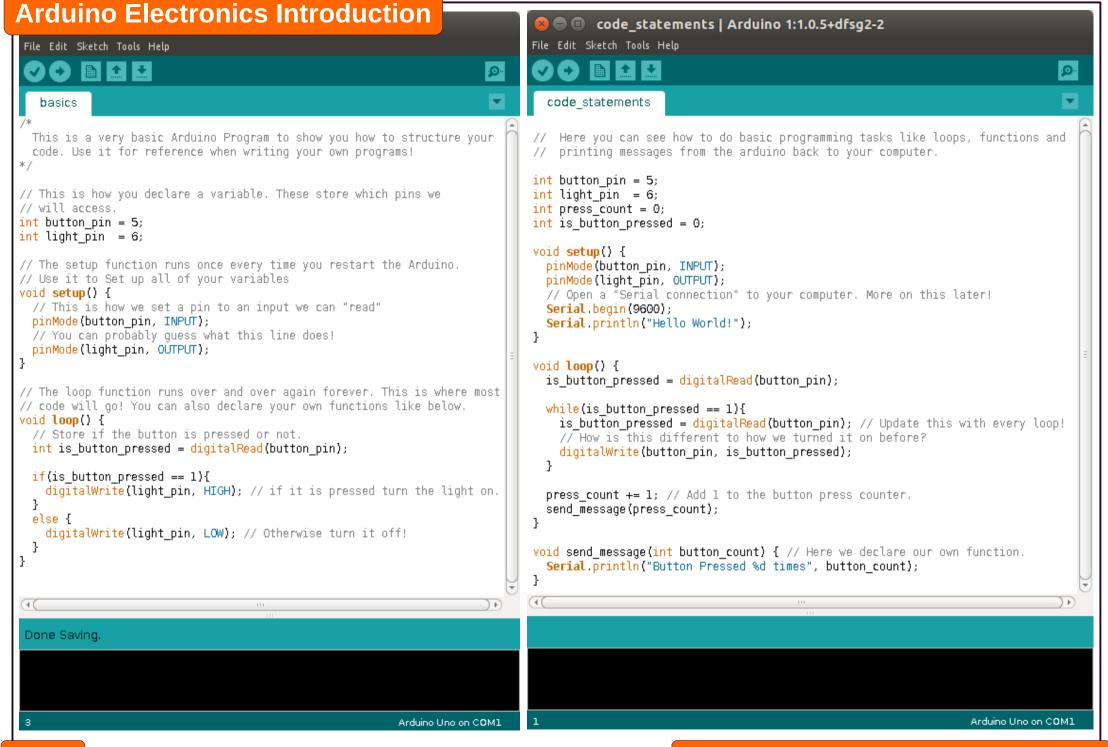5) Program the board!

Click on the button with the arrow pointing right under "Edit". This will compile your code and "upload" it to the Arduino! When it finishes, you should see a single LED on the board flashing on and off. Congratulations, you now know how to program and Arduino!







LED's and Resistors


These are the two most basic components we can use. Try copying this circuit and controlling the LED with the Button and the Arduino. The long leg of the LED always connects to power.

We always use a resistor with an LED.

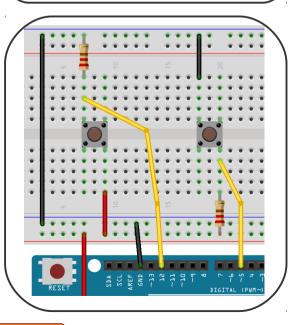This makes sure it doesn't draw too much power and burn out!



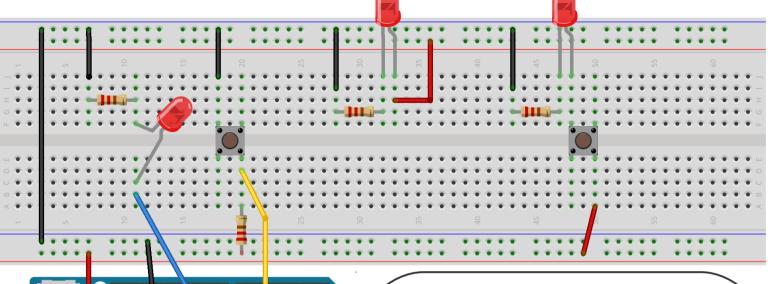

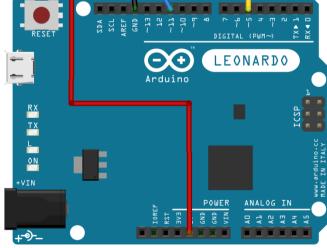

Try building the circuit on the left. What do you notice is different about the values the buttons normally take? Print them out so you can see them.

Here is the code you will need, can you work out where to put it all?

```
digital_read_write

// Declare a variable to store the button
int button_pressed;
// Read the value of the pin with the button
button_pressed = digitalRead(<pin number>);

// Turn on an output pint
digitalWrite(<pin number>, HIGH);
// Or turn off an output pin
digitalWrite(<pin number>, LOW);

// if statement
if(<my variable> == <some value>){
    // DO something!
}
else {
    // DO something ELSE!
}
```


Potentiometers

These are *variable* resistors, but we can change how much "resistance" they have. Think of them as sliding scales we can use to control things. In this circuit, we can control the brightness of an LED or the position of a servo arm. They have three pins. Left for ground, right for power and the middle to the Arduino analogue inputs.

Servo's

Our first mechanical output. They have an "arm" that moves back and forth depending on how we control it. They have three wires. One for power (red), one for ground (black) and the yellow one we connect to the Arduino. Make sure you use a pin with a ~ next to it!

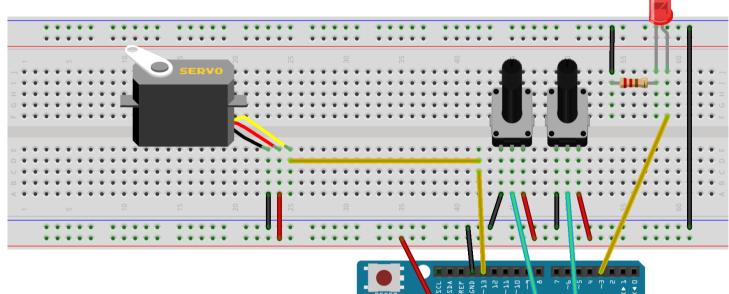
The way we read the value of the potentiometer is the same for all analogue inputs. So, the same could work for microphones or light sensors. Can you make an LED that gets brighter as the room darkens?




```
// We need this line to use the servo!
#include "servo.h"
                                                                            LEO ARDO
// We will use this variable to control the servo
Servo my servo;
void setup() {
  // Associate the pin with our servo variable
  mv servo.attach(<servo pin>);
void loop() {
 // Read and store analogue input zero.
 int pot 1 = analogRead(A0):
 // For more info on the "map" function, look at the arduino reference page.
 int toWrite = map(pot 1, 0, 1023, 0, 180);
                                  // Move the servo arm!
 my servo.write(toWrite);
 analogWrite(<LED pin>, toWrite); // Set the brightness of the LED
```

fritzing

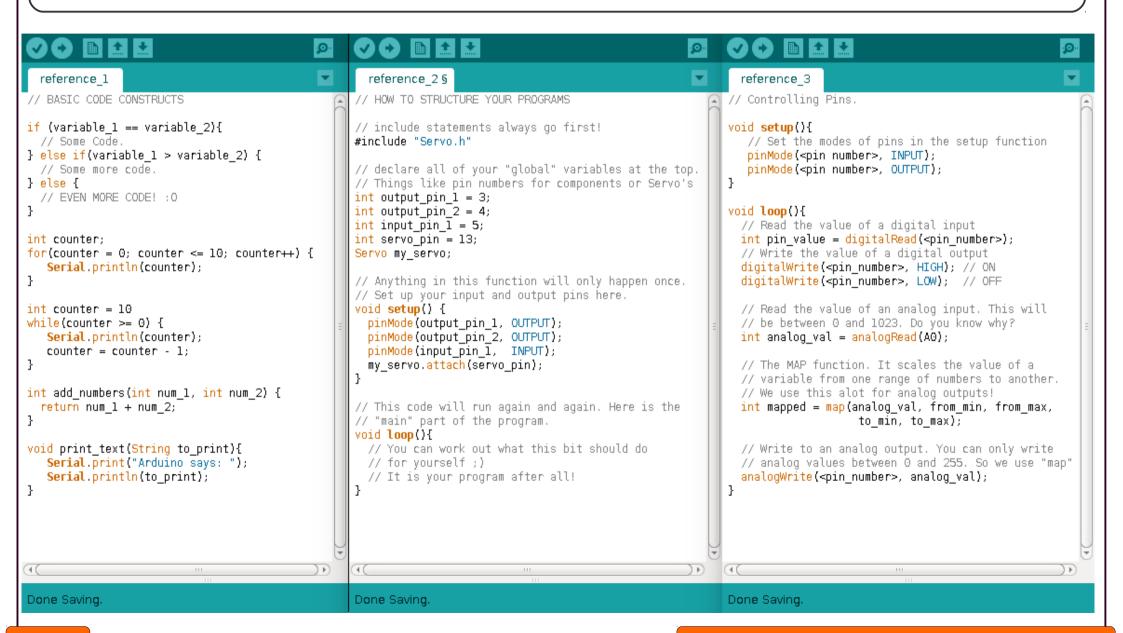This page has some reference code to help you with writing the programs for the Arduino. Please do ask if something doesn't make sense! You can also look on http://arduino.cc/en/Reference for more



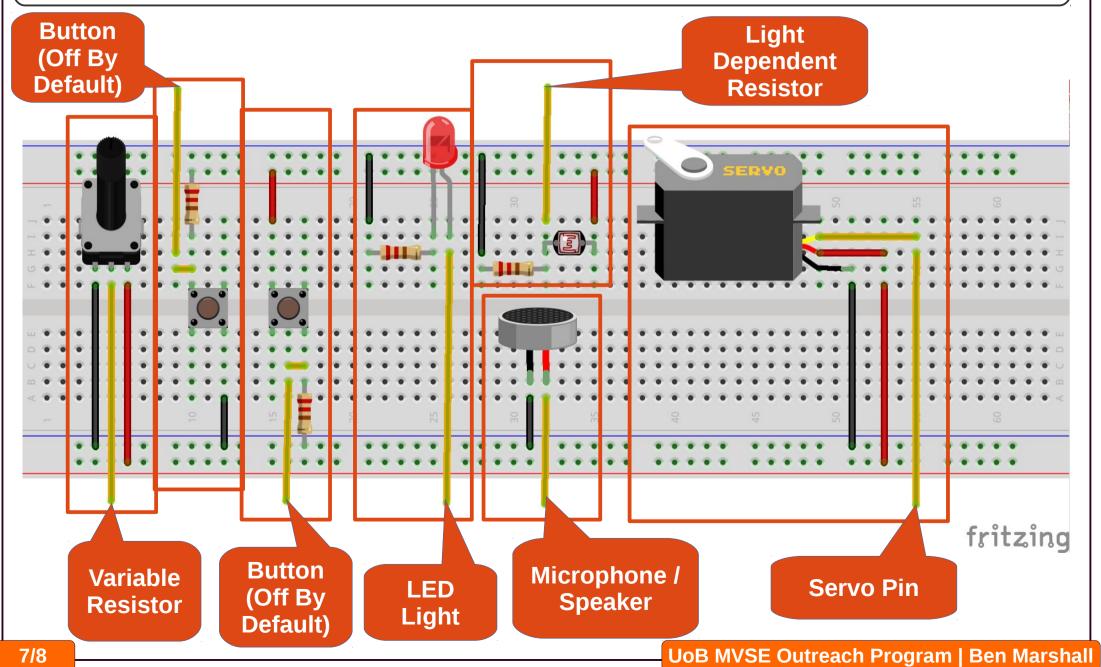This page has example diagrams for how to connect different types of component to the Arduino. You can use several of these circuits on the breadboard with the Arduino to make almost anything!



Scratch pad: Use this page for your own notes and diagrams. It helps to draw a circuit to get it clear in your head before trying to build it!

More Materials:

Arduino Website: http://arduino.cc Project Ideas: http://instructables.com

Contact: ben@bmarshall.org.uk outreach@cssbristol.co.uk